

Total No. of Questions : 4]

SEAT No. :

P8563

[Total No. of Pages : 2

Oct-22/TE/Insem-534

T.E. (Electrical)

POWER ELECTRONICS

(2019 Pattern) (Semester - I) (303142)

Time : 1 Hour]

[Max. Marks : 30

Instructions to the candidates:

- 1) Answer Q1 or Q2, Q3 or Q4.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Assume suitable data if necessary.

Q1) a) State and explain different modes of operation of SCR with the help of V-I characteristics. **[5]**

b) Explain the triggering of SCR using RC gate triggering. **[5]**

c) Explain the following specifications of Thyristor - **[5]**

i) dv/dt

ii) di/dt

iii) VGT

iv) VRRM

v) IT (RMS)

OR

Q2) a) With neat constructional diagram explain working of GTO. Draw its V- I Characteristic. **[5]**

b) What is commutation? Explain class C commutation of SCR. **[5]**

c) With neat circuit diagram explain how overcurrent protection provided to Thyristor. **[5]**

P.T.O.

- Q3)** a) Explain first quadrant chopper. How these choppers can be used to obtain two quadrant choppers? [5]
- b) Draw and explain output and transfer characteristics of MOSFET. [5]
- c) What is the duty cycle of chopper and explain PWM and FM techniques of voltage control. [5]

OR

- Q4)** a) Explain class 'B' chopper with neat circuit diagram. Draw output voltage & output current waveforms. [5]
- b) Describe the principle of step up chopper. Derive an expression for average output voltage in terms of input voltage and duty cycle. [5]
- c) A step up chopper has input voltage of 220 V and output voltage of 660V. If the conducting time of chopper is 100μsec, calculate the pulse width of output voltage. [5]

