

Total No. of Questions : 8]

SEAT No. :

**P289**

[Total No. of Pages : 3

[6003]-368

**T.E. (Electrical)**

**POWER SYSTEM-II**

**(2019 Pattern) (Semester-II) (303148)**

*Time : 2½ Hours]*

*[Max. Marks : 70*

*Instructions to the candidates:*

- 1) Answer Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8.
- 2) Neat diagram must be drawn wherever necessary.
- 3) Figures to the right side indicate full marks.
- 4) Use of a calculator is allowed.
- 5) Assume suitable data if necessary.

- Q1)** a) Give the detailed classification of buses used in load flow analysis. [6]
- b) State the following statements are true or false with justification. [6]
- i) The bus admittance matrix is a sparse matrix
  - ii) In fast decoupled load flow, the resistance of the lines are neglected.
- c) Impedances (in pu) between buses are given in the following Fig. Calculate the Ybus of the system. [6]



Fig Q1(c)

OR

- Q2)** a) Draw the per-unit impedance diagram of the system shown below. Take the base values as 10MVA, 33kV on the load [6]

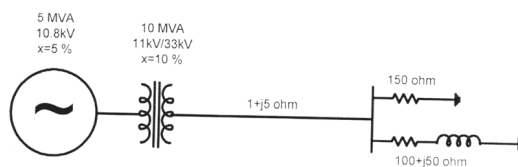


Fig Q2A)

**P.T.O.**

- b) Explain load flow analysis using the fast decoupled method. [6]
- c) What is per unit system? State the advantages and disadvantages. [6]

**Q3) a)** For the power system shown in the figure below, the specifications of the components are the following: [12]

G1 : 25kV, 100 MVA,  $X=9\%$  G2: 25kV, 100 MVA,  $X=9\%$

T1 : 25kV/220 KV, 90 MVA,  $X=9\%$  T2: 220 kV/25kV, 90MVA,  $X=9\%$

Line 1:  $X=150$  ohms

If the three-phase fault is taken place at bus 1, calculate fault current supplied by each generator. Take generator 1 rating as base values.

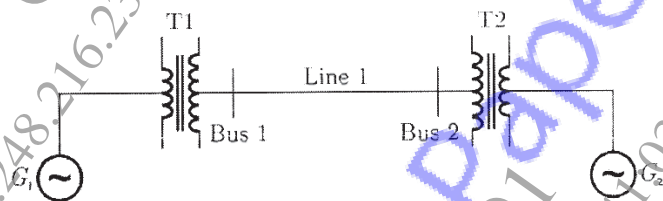


Fig. Q3A)

- b) Draw the nature of fault current, if the symmetrical fault is taken place at the terminal of an unloaded alternator. Clearly mark the sub-transient, transient and steady state period. [6]

OR

**Q4) a)** Find the fault current, if three phase fault is taken place at (i) F1 and (ii) F2. [12]

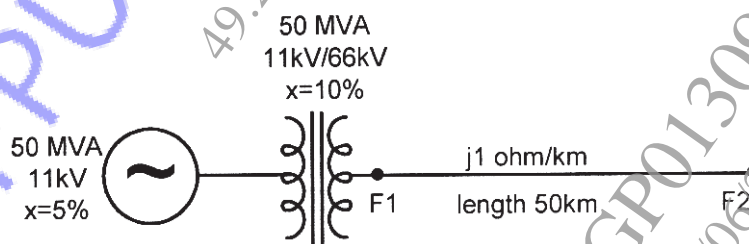


Fig Q4A)

- b) Write a short note on "Feeder reactor". [6]

**Q5) a)** With usual notation, prove that three-phase apparent power. [6]

$$S_{abc} = 3(V_{a1} I_{a1}^* + V_{a2} I_{a2}^* + V_{a0} I_{a0}^*)$$

**b)** Draw a zero-sequence diagram for the following transformer connection. [6]

i) Delta-star transformer (With isolated neutral)

ii) Delta-star connected transformer with neutral grounded with impedance

**c)** For a transmission line, positive sequence impedance is  $(1+j10)$  ohm and zero sequence impedance is  $(4+j31)$  ohm. Determine following matrix where  $Z_s$  = Self impedance and  $Z_m$  is mutual impedance of the transmission line. [6]

$$Z_{line} = \begin{bmatrix} Z_s & Z_m & Z_m \\ Z_m & Z_s & Z_m \\ Z_m & Z_m & Z_s \end{bmatrix}$$

OR

**Q6) a)** Derive the equation for fault current in LLG fault. [9]

**b)** A 20-MVA, 6.6-kV, 3-Phase alternator is connected to a 3-Phase transmission line. The per unit positive, negative and zero-sequence impedances of the alternator are  $j0.1$ ,  $j0.05$  and  $j0.04$  respectively. The neutral of the alternator is connected to the ground through an inductive reactor of  $j0.05$  p.u. The per unit positive, negative and zero-sequence impedances of the transmission line are  $j0.2$ ,  $j0.2$  and  $j0.3$ , respectively. Per-unit values are based on the machine ratings. A solid ground fault occurs at one phase of the far end of the transmission line. Calculate the fault current. [9]

**Q7) a)** Compare HVDC and EHVAC transmission systems. [6]

**b)** Draw the complete single-line diagram of the HVDC system showing all components. [5]

**c)** Write a short note "Monopolar HVDC station". [5]

OR

**Q8) a)** Explain "Constant Extinction Angle control in HVDC systems" [6]

**b)** Write the functions of the following components in HVDC system: [5]

i) AC side filters.

ii) Converter transformer.

**c)** Write a short note "Chandrapur-Padghe HVDC line". [5]